

Report: DC Motor Control using Arduino UNO + L293D

1. Objective

To design, wire, and simulate a single DC motor control system using Arduino UNO and the L293D H-bridge motor driver. The system demonstrates bidirectional control (forward/backward) and speed control using PWM. This report documents the procedure, wiring with color codes, pin-to-pin mapping, and the mathematical model for PWM control.

2. Components

Component	Quantity	Notes
Arduino UNO	1	Controller (5V logic)
L293D IC	1	H-bridge motor driver
DC Motor	1	6–9V rated
Battery	1	6–9V motor supply
Breadboard	1	For interconnections
Jumper Wires	As needed	Color-coded wiring

3. Step-by-Step Procedure

- Place the L293D across the breadboard center gap so pins on each side are isolated.
- Connect common ground: Battery (–), Arduino GND, and L293D GND pins must share the same ground rail.
- Provide logic power: Arduino 5V → L293D Pin 16 (Vcc1).
- Provide motor power: Battery (+) → L293D Pin 8 (Vcc2).
- Connect motor outputs: L293D Pins 3 & 6 → DC Motor terminals.
- Connect control pins: IN1 → Arduino D8, IN2 → Arduino D9.
- Enable pin for PWM speed: EN1 → Arduino D6 (PWM).
- Upload the sketch and verify motion in simulation/Serial Plotter.

4. Wiring Map (Pin-to-Pin with Color Codes)

Wire Color	From (Arduino / Battery)	To (L293D / Motor)	Purpose
Green	Arduino GND / Battery (–)	Pins 4, 5, 12, 13 (GND)	Common ground
Blue	Arduino 5V	Pin 16 (Vcc1)	Logic power
Red	Battery (+)	Pin 8 (Vcc2)	Motor supply
Orange	Arduino D8	Pin 2 (IN1)	Direction control A
Orange	Arduino D9	Pin 7 (IN2)	Direction control B
Purple	Arduino D6 (PWM)	Pin 1 (EN1)	Speed control (PWM)
Black	Motor lead	Pin 3 (OUT1)	Motor output
Black	Motor lead	Pin 6 (OUT2)	Motor output

5. L293D Pin Map (Top View)

Pin numbering (Top View):

- 1 EN1 16 Vcc1 (Logic +5V)
- 2 IN1 15 IN4

3 OUT1 14 OUT4
4 GND 13 GND
5 GND 12 GND
6 OUT2 11 OUT3
7 IN2 10 IN3
8 Vcc2 9 EN2

6. Mathematical Model (PWM Speed Control)

Arduino PWM uses an 8-bit duty cycle. The `analogWrite(value)` maps $\text{value} \in [0, 255]$ to duty cycle $D = \text{value}/255$. Motor voltage (average) approximates: $V_{\text{avg}} \approx D \times V_{\text{motor_supply}}$. Example: For $\text{value} = 180$ and $V_{\text{motor_supply}} = 9\text{V}$, $D = 180/255 \approx 0.706 \rightarrow V_{\text{avg}} \approx 6.35\text{V}$. Direction is set by IN1/IN2: (HIGH, LOW) $\rightarrow$ Forward; (LOW, HIGH) $\rightarrow$ Reverse; (LOW, LOW) $\rightarrow$ Stop; (HIGH, HIGH) $\rightarrow$ Brake.

7. Direction Truth Table

IN1	IN2	Result
HIGH	LOW	Forward
LOW	HIGH	Backward
LOW	LOW	Stop (Coast)
HIGH	HIGH	Brake

8. Safety & Notes

- Always keep common ground between Arduino, L293D, and battery.
- Do not feed 9V into Arduino 5V pin. Use VIN/DC jack only if powering Arduino externally.
- 9V block batteries are weak for motors; prefer AA packs or Li-ion for real hardware.
- Ensure EN1 is driven HIGH or PWM; otherwise the motor will not spin.